

#Jenny



Finally I get this ebook, thanks for all these I can get now!

#Rio



Cool! I'am really happy

#Markus Jensen



I did not think that this would work, my best friend showed me this website, and it does! I get my most wanted eBook

#Hun Tsu



wtf this great ebook for free?!

#Che Salsa



My friends are so mad that they do not know how I have all the high quality ebook which they do not!

#Diego Butler



so many fake sites. this is the first one which worked! Many thanks

Schaumann: Design of Analog Filters  
Chapter 1: Introduction

Introduction 1-1

1.1 The gain  $G = 20 \log_{10}(V_2) = 20 \log_{10}(3.3) = 14.55$  dB  
Phase shift  $\Delta \phi = \theta_2 - \theta_1 = 180^\circ - 125.7^\circ$

1.2 At 12 kHz, the gain of the filter is  $G = 10^{14.55/20} = 1.219 \times 10^4$   
 $\Rightarrow$  The amplitude of output signal is  $V_2 = V_1 \times 1.219 \times 10^4 = 125.9$   $\mu$ V.

1.3  $\sigma = 20 \log_{10}(1 \times 10^{-3}) - 20 \log_{10}(2.5 \times 10^{-7}) = -66.94$  dB

1.4 The gain is  $G = 10^{14.55/20} = 1.219 \times 10^4$ ,  $Z = 56.25 \angle -42^\circ$ , hence the output signal is  
 $V_2 = V_1 \times 1.219 \times 10^4 \times 0.62 \angle -42^\circ = 151.6 \angle -42^\circ$   
 $\Rightarrow V_2(t) = 151.6 \cos(\omega t - 42^\circ)$

1.5 (a) Lowpass. Transition bandwidth  $BW_{tr} = 9.8 - 3.4 = 6.2$  kHz  
(b) Bandpass. Transition bandwidth  $BW_{tr} = 12.5 - 7 = 5.5$  kHz,  $BW_{bp} = 40 - 24 = 16$  kHz  
(c) Bandstop. Transition bandwidth  $BW_{tr} = 12.5 - 7 = 5.5$  kHz,  $BW_{bs} = 40 - 24 = 16$  kHz  
(d) Highpass. Transition bandwidth  $BW_{tr} = 40 - 24 = 16$  kHz  
(e) Lowpass. Transition bandwidth  $BW_{tr} = 600 - 300 = 240$  kHz  
(f) Bandpass. Transition bandwidth  $BW_{tr} = 1000 - 700 = 270$  kHz,  $BW_{bp} = 7.8 - 2.4 = 5.4$  MHz

1.6 At  $\omega_c = 0$ , hence the gain is  $20 \log_{10}(1) = 20 \log_{10}(0.32) = -20 \log_{10}(3.125) = -25.41$  dB  
At high frequencies  $|T(j\omega)|_{\omega \rightarrow \infty} = \sigma^2$ , attenuation  $a(\omega) = 20 \log_{10}(\sigma^2) = -40 \log_{10}(\sigma)$  increases  
40 dB per decade.  
When  $\omega = \infty$  (infinite), attenuation is infinite.

1.7 In this problem's solution, denormalized component values are denoted by "a".  
Denormalized parameters are  $R_1 = R_2 = R_3 = 1 \text{ k}\Omega$ ,  $L = \frac{1}{s} \text{ H}$ , and  $C = C_1(sR_1)$ , therefore  $R_1 = 300$   
 $\Omega$ ,  $R_2 = 300 \text{ k}\Omega$ ,  $L = 5.547 \text{ }\mu\text{H}$ ,  $L_2 = 4.385 \text{ }\mu\text{H}$ ,  $L_3 = 3.875 \text{ }\mu\text{H}$ ,  $C_1 = 126.0 \text{ pF}$ ,  $C_2 = 77.44 \text{ pF}$

1.8 In this problem's solution, denormalized component values are denoted by "a". Since  
denormalized capacitance is  $C = C_1(sR_1)$ , where  $R_1$  is the normalization resistor, we have  
 $R_1 = \frac{1}{sC} = \frac{1}{s \times 0.5 \text{ nF}} = 2 \times 10^9 \times 10^9 \text{ }\Omega$   
Therefore the denormalized resistors are  
 $R_1 = R_2 = R_3 = 1.243 \times 10^9 \times 10^9 = 8.408 \text{ k}\Omega$   
 $R_4 = R_5 = R_6 = 1.677 \times 10^9 \times 10^9 = 11.343 \text{ k}\Omega$   
 $R_7 = R_8 = 8.888 \times 10^8 \times 10^9 = 46.59 \text{ k}\Omega$

Copyright Oxford University Press

[Download PDF version of :](#)  
**Analog Filters Schaumann Solution Manual Book**